
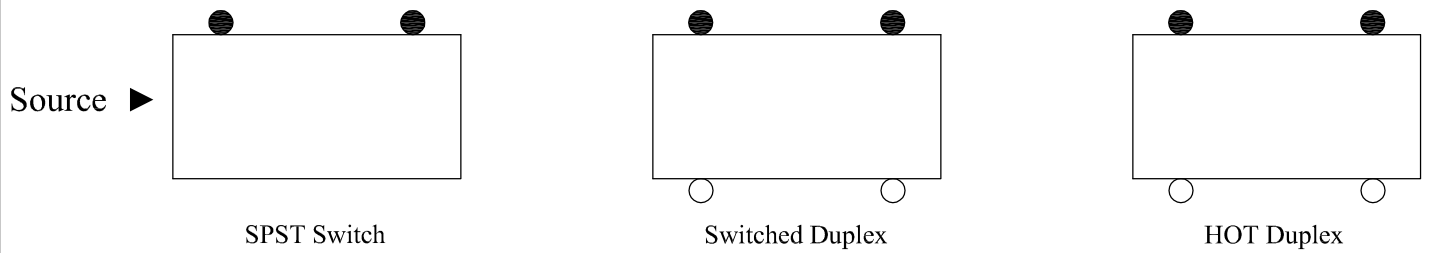


Circuit Diagramming Exercises


3. Simple Circuit with a HOT Duplex

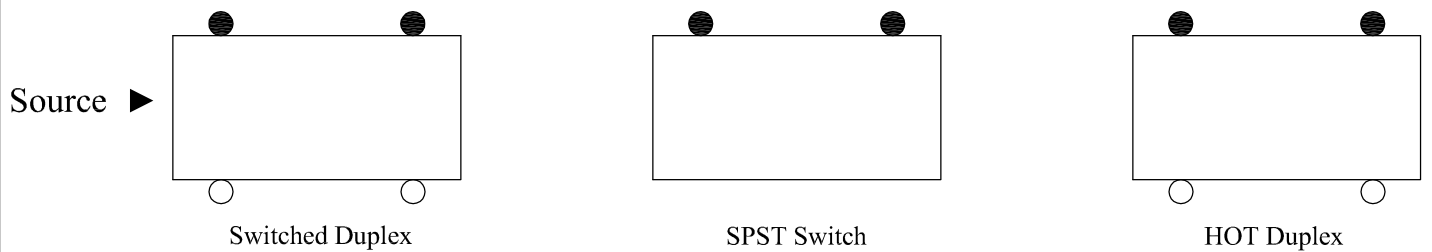

4. Switch Loop Circuit with a HOT Duplex



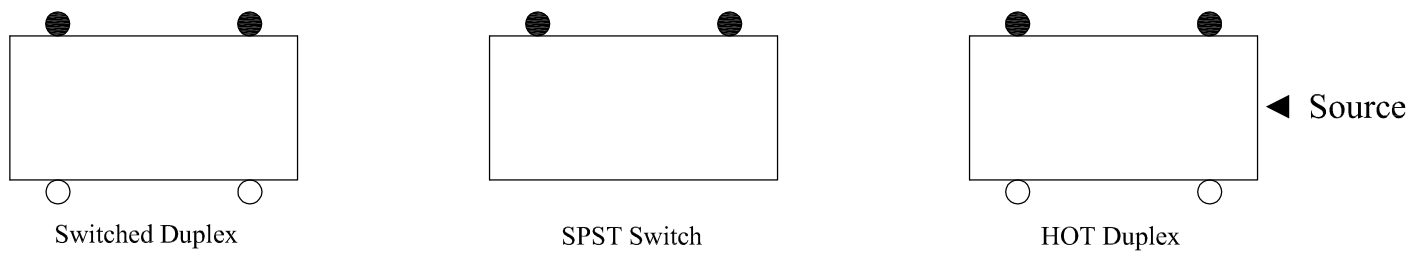5. HOT Duplex with a Simple Switch Circuit



6. 3-Way Circuit #1

